

## TIMING

In timing circuits you are controlling the rate of response of the capacitor or controlling the rate of the voltage across the capacitor.


The simplest timing circuit is a series combination of a resistor and capacitor. The time constant is the amount of time to charge the capacitor to 63% of the input voltage and is equal to the resistance times the capacitance ( $T = RC$ ). By changing the values of the resistance and capacitance, you can have time constants ranging from microseconds to weeks. The important capacitor characteristics are:

- ESR
- Insulation resistance
- Capacitance change vs. time
- Capacitance change vs. temperature

Typical charge and discharge voltage waveforms are shown below.



### CHARGING CIRCUIT

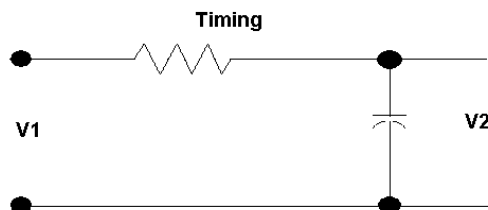

$V(2)$  is the voltage across the capacitor after time  $T_n$  expressed mathematically

$$V(2) = V(1)(1 - e^{-T_n/T_c})$$

$$T_n = CR \ln \frac{V(1)}{V(1) - V(2)}$$

$T_c = RC$  time constant


$R$  = series resistance

$C$  = capacitance

$V(1)$  = applied voltage

In an actual timing circuit, the leakage current must be considered since it will adversely affect the circuit.

**Actual Charging Circuit**

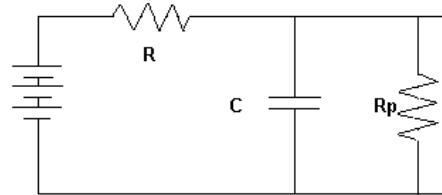

$$T_n = K CR \ln \frac{KV}{KV - V(2)}$$

Where  $K = \frac{R_p}{R+R_p}$  and  $R_p =$  leakage resistance

### DISCHARGE CIRCUITS

During discharge, the voltage across the capacitor after time  $T_n$  is

$$V(2) = V e^{-T/T_c}$$

$$T_n = CR \ln [V(1)/V(2)]$$

When the leakage current is factored in the discharge equation becomes:

$$T_n = K CR \ln [KV(1)/V(2)]$$

Where  $K = \frac{R_p}{R + R_p}$

It becomes very evident that a capacitor with a high amount of leakage current can cause the time constant of the circuit to get longer than desired.